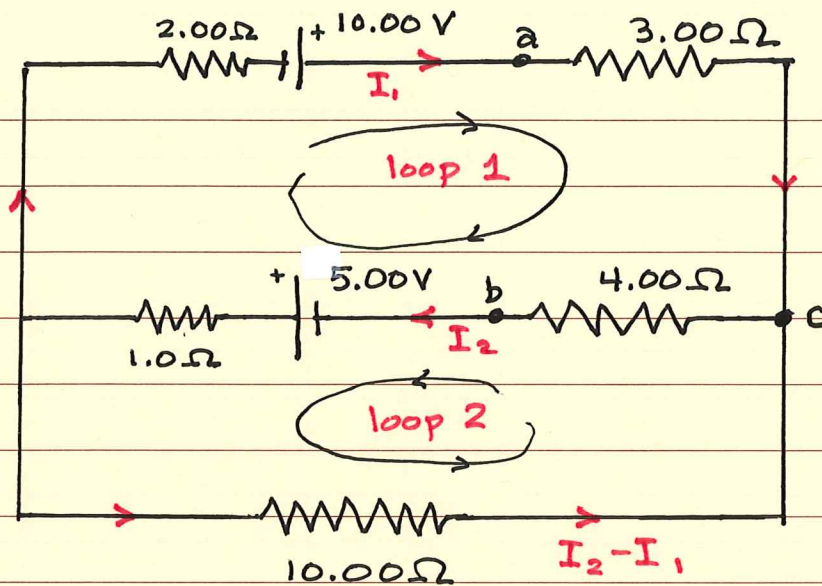


PS250 Homework Problem 26.29

DATE	
TOPIC	



Loop 1: $\sum V_i = 0 \quad -I_1(2\Omega) + 10V - I_1(3\Omega) - I_2(4\Omega) + 5.0V - I_2(1\Omega) = 0$
 $-(5\Omega)I_1 - (5\Omega)I_2 + 15V = 0$

$(1) \quad (5\Omega)I_1 + (5\Omega)I_2 = 15V$

Loop 2: $\sum V_i = 0 \quad -I_2(4\Omega) + 5.0V - I_2(1\Omega) - (I_2 - I_1)(10\Omega) = 0$
 $(10\Omega)I_1 - (15\Omega)I_2 + 5V = 0$

$(2) \quad -(10\Omega)I_1 + (15\Omega)I_2 = 5V$

$2 \times (1) \rightarrow (10\Omega)I_1 + (10\Omega)I_2 = 30V$
 $(2) \rightarrow -(10\Omega)I_1 + (15\Omega)I_2 = 5V$

$I_2 = \frac{7}{5} A$

Sum $\rightarrow 0 I_1 + (25\Omega)I_2 = 35V$ $(1) \rightarrow (5\Omega)I_1 + (5\Omega)\left(\frac{7}{5} A\right) = 15V$

$(5\Omega)I_1 = 15V - 7V = 8V$ $I_1 = \frac{8}{5} A$ $I_2 - I_1 = -\frac{1}{5} A$

b.) $V_{ab} = V_{ac} + V_{cb} = I_1(3\Omega) + I_2(4\Omega) = \left(\frac{8}{5} A\right)3\Omega + \left(\frac{7}{5} A\right)4\Omega$

$V_{ab} = \left(\frac{24}{5} + \frac{28}{5}\right) \text{ volts}$ $V_{ab} = \frac{52}{5} V$ $V_{ab} = 10.4 \text{ volts}$