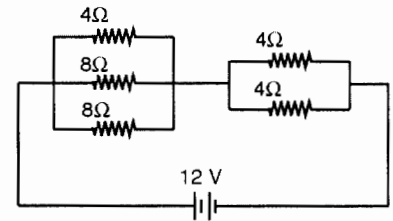


Show your work !!

10 points

1. A resistor network is connected to a 12-V battery as shown in the figure to the right.

Answer Key
Name _____



a. Calculate the equivalent resistance.

$$\left. \begin{aligned} \frac{1}{8} + \frac{1}{8} + \frac{1}{4} &= \frac{1}{2} \Rightarrow 2\Omega \\ \frac{1}{4} + \frac{1}{4} &= \frac{1}{2} \Rightarrow 2\Omega \end{aligned} \right\} 2\Omega + 2\Omega = 4\Omega$$

$R_{eq} = \underline{4} \Omega$

b. Calculate the current supplied by the battery.

$$I = \frac{V}{R} = \frac{12V}{4\Omega} = 3A$$

$I_{battery} = \underline{3} A$

c. Calculate the power supplied by the battery.

$$P = VI = (12V)(3A) = 36 \text{ Watts}$$

$P_{battery} = \underline{36} W$

d. Calculate the current in one of the 8Ω resistors.


$$I = \frac{V}{R} = \frac{6 \text{ volts}}{8\Omega} = 0.75 A$$

$I_{8\Omega} = \underline{0.75} W$

15 points

2. Applying Kirchhoff's rules to following circuit, calculate the following:

Hint: one of the currents is zero.

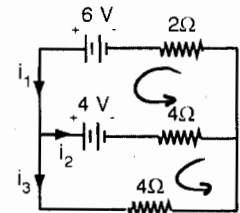

a. Calculate the currents i_1 , i_2 , and i_3 .

$$i_1 = i_2 + i_3$$

Top loop: $6V - 4V - 4i_2 - 2i_1 = 0$

Bottom loop: $4V - 4i_3 + 4i_2 = 0$

Top: $2V = 2i_1 + 4i_2$

Bottom: $4V = -4i_2 + 4i_3$

Top: $-4V = -12i_2 - 4i_3$

Bottom: $4V = -4i_2 + 4i_3$

$$0 = -16i_2$$

$i_2 = 0$

$i_1 = i_3$

Top: $2V = 6 \times 0 + 2i_3$

$i_3 = 1$

$i_1 = \underline{1} A$

$i_2 = \underline{0} A$

$i_3 = \underline{1} A$

b. Calculate the power delivered by the two batteries.

$$P_{6V} = (6V)(1A) = 6W$$

$P_{6V} = \underline{6} W$

$$P_{4V} = (4V)(0A) = 0W$$

$P_{4V} = \underline{0} W$

c. Show that the power dissipated by the resistors equals the total power supplied by the batteries.

$$i_1^2 (2\Omega) = 2W$$

$$i_2^2 (4\Omega) = 0W$$


$$i_3^2 (4\Omega) = 4W$$

Total Power Dissipated = 6W

Same as the power supplied by the battery.

15 points

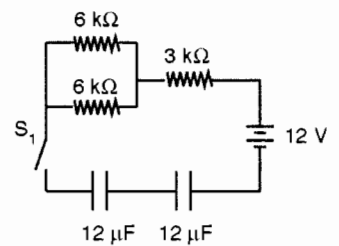3. An RC circuit is shown in the figure to the right. The capacitors are initially uncharged. The switch S_1 is closed at $t = 0$ and the capacitors begin to charge.



$$R_{eq} = \left(\frac{1}{6k\Omega} + \frac{1}{6k\Omega} \right)^{-1} + 3k\Omega = \underline{6k\Omega}$$

$$C_{eq} = \left(\frac{1}{12\mu F} + \frac{1}{12\mu F} \right)^{-1} = \underline{6\mu F} \quad \tau = RC = (6k\Omega)(6\mu F)$$

$$\tau = \underline{36ms}$$

$$\tau = \underline{36} \text{ ms}$$

b. Find the total charge stored on the capacitors once they have become completely charged.

$$Q = VC_{eq} = 12V (6\mu F) = \underline{72\mu C}$$

$$Q_{total} = \underline{72} \mu C$$

c. Find the initial current immediately after S_1 is closed.

$$I_0 = \frac{V}{R_{eq}} = \frac{12V}{6 \times 10^3 \Omega} = \underline{2mA}$$

$$I_0 = \underline{2} \text{ mA}$$

d. Find the current at 72 ms.

$$I = I_0 e^{-t/RC} = 2mA e^{-72/36} = 2mA (e^{-2}) = \underline{0.271mA}$$

$$I = \underline{0.271} \text{ mA}$$

e. What is the instantaneous power supplied by the battery at $t = 72ms$?

$$P = VI = (12V)(0.271 \times 10^{-3}A) = 3.25 \times 10^{-3} \text{ watts}$$

$$= \underline{3.25mW}$$

$$P = \underline{3.25} \text{ mW}$$

I from part d

10 points

4. Protons enter a velocity selector shown in the figure to the right. The electric and magnetic fields in the velocity selector are 1.00×10^6 V/m and 1.00 T.

a. Calculate the velocity of the protons exiting the velocity selector.

$$\vec{F} = q(\vec{E} + \vec{v} \times \vec{B}) = \vec{0} \text{ for protons traveling in a straight line.}$$


$$v = \frac{E}{B} = \frac{1.00 \times 10^6 \text{ V/m}}{1.00 \text{ T}} = 10^6 \text{ m/s}$$

$$v = \underline{10^6} \text{ m/s}$$

b. After leaving the velocity selector, the protons enter region containing a constant, homogeneous magnetic field of 0.1042 T. Find the radius of curvature of the protons as they begin to orbit in the magnetic field.


$$R = \frac{mv}{qB} = \frac{(1.67 \times 10^{-27} \text{ kg})(10^6 \text{ m/s})}{(1.602 \times 10^{-19} \text{ C})(0.1042 \text{ T})} = 0.100 \text{ m}$$

$$R = \underline{10} \text{ cm}$$

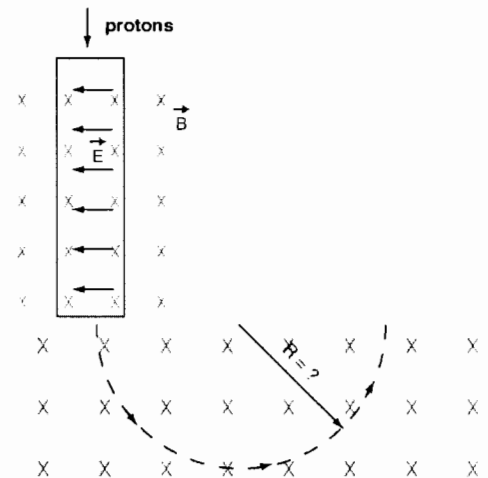

15 points

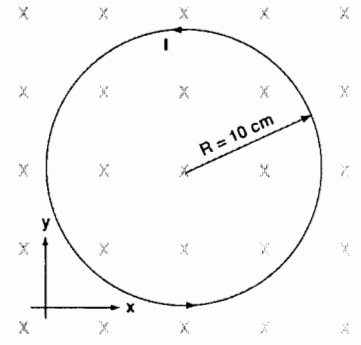5. A current loop 10 cm in radius carries a current of 2.00 A as shown in the figure to the right.



a. Calculate its magnetic dipole moment.

$$\mu = IA = (2.00 \text{ A}) \pi (0.100 \text{ m})^2 = 6.28 \times 10^{-2} \text{ A}\cdot\text{m}^2$$

$$\mu = 6.28 \times 10^{-2} \text{ A}\cdot\text{m}^2$$

b. The current loop is inserted in a homogenous magnetic field of 1.30 T and is initially in its "highest" potential energy orientation. How much work is done by the magnetic field to "flip" the magnetic dipole moment 180° to its "lowest" potential energy orientation?

$$W = -\Delta U = -(U_f - U_i) = -(-\mu \cdot B \cos \theta_f - (-\mu B \cos \theta_i))$$

$$W = \mu B (\cos \theta_f - \cos \theta_i) = \mu B (\cos 0^\circ - \cos 180^\circ) = 2\mu B$$

$$W = 2(6.28 \times 10^{-2} \text{ A}\cdot\text{m}^2)(1.30 \text{ T}) = 0.163 \text{ J}$$

$$W_{\text{mag field}} = 0.163 \text{ J}$$

c. What is the maximum torque applied to the magnetic dipole while it is "flipping" from its initial position to its final position? This occurs when $\theta = 90^\circ$

$$\vec{\tau} = \vec{\mu} \times \vec{B} \quad \tau = \mu B \sin \theta = \mu B \sin 90^\circ = \mu B = (6.28 \times 10^{-2})(1.30)$$


Note: There's an ambiguity in the direction of the torque. It could be in either $+\hat{j}$ or $-\hat{j}$ direction.

$$\vec{\tau} = (0 \hat{i} + 8.17 \times 10^{-2} \hat{j} + 0 \hat{k}) \text{ N}\cdot\text{m}$$

10 points

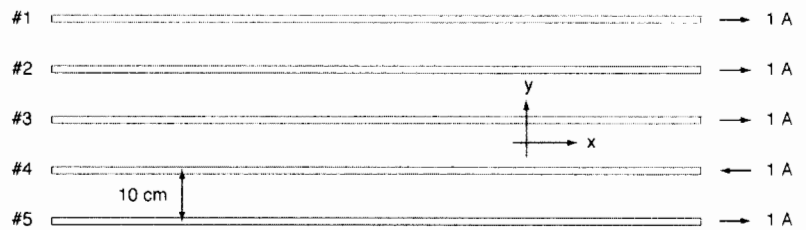6. Currents are flowing through infinitely-long, equally-spaced, parallel wires as wires shown in the figure to the right.

$$F = ILB = IL \frac{\mu_0 I}{2\pi R} \quad \frac{F}{L} = \frac{\mu_0 I^2}{2\pi R}$$



a. Calculate the force per unit length on wire #2.

$$\left(\frac{F}{L} \right)_2 = + \frac{\mu_0 I^2}{2\pi(0.20)} - \frac{\mu_0 I^2}{2\pi(0.30)} = \frac{\mu_0 I^2}{2\pi} \left(\frac{1}{0.2} - \frac{1}{0.3} \right)$$

$$2 \times 10^{-7} (1)^2 (1.67) = 3.33 \times 10^{-7} \text{ (upward)}$$

$$F/L = +3.33 \times 10^{-7} \hat{j} \text{ N/m}$$

b. Calculate the force per unit length on wire #4.

$$\left(\frac{F}{L} \right)_4 = \frac{\mu_0 I^2}{2\pi(0.20)} + \frac{\mu_0 I^2}{2\pi(0.30)} = \frac{\mu_0 I^2}{2\pi} \left(\frac{1}{0.2} + \frac{1}{0.3} \right)$$

$$2 \times 10^{-7} (1)^2 (8.33) = 1.67 \times 10^{-6} \text{ (downward)}$$

$$F/L = -1.67 \times 10^{-6} \hat{j} \text{ N/m}$$

c. Calculate the force per unit length on wire #3.

$$\left(\frac{F}{L} \right)_3 = \frac{\mu_0 I^2}{2\pi(0.10)} + \frac{\mu_0 I^2}{2\pi(0.10)} = \frac{\mu_0 I^2}{2\pi} \left(\frac{2}{0.10} \right) = \frac{2 \times 10^{-7} (1)^2 2}{0.10} = 4 \times 10^{-6} \text{ (upward)}$$

$$F/L = 4 \times 10^{-6} \hat{j} \text{ N/m}$$

(#1 and #5 cancel)