

Show your work !!

Answer Key

Name _____

10 points

1. A strand of wire has resistance $5.60 \mu\Omega$. Find the net resistance of 120 such strands if they are:

a) placed side by side to form a cable of the same length as a single strand.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_{120}} = \frac{N}{R} \quad R_{eq} = \frac{R}{N} = \frac{5.60 \mu\Omega}{120} = 4.67 \times 10^{-8} \Omega$$

$R = 4.67 \times 10^{-8} \Omega$


b) connected end to end to form a wire 120 times as long as a single strand.

$$R_{eq} = R_1 + R_2 + R_3 + \dots + R_{120} = NR = 120(5.60 \mu\Omega) = 6.72 \times 10^{-4} \Omega$$

$R = 6.72 \times 10^{-4} \Omega$

15 points

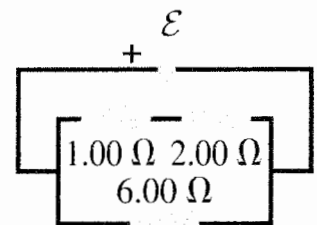2. A resistor circuit is shown in the figure to the right. The voltage across the 2.00Ω is 12.0 V .



emf = 18.0 volts

a. What is the emf of the battery?

$$i_{2\Omega} = \frac{V}{R_{2\Omega}} = \frac{12 \text{ V}}{2 \Omega} = 6 \text{ A} \quad V_{drop}(1\Omega) = IR_{1\Omega} = 6 \text{ A}(1\Omega)$$

$$V_{drop}(1\Omega) = 6 \text{ volts}$$

$$\mathcal{E} = 12 \text{ V} + 6 \text{ V} = 18 \text{ V}$$

b. What is the current in the 1.00Ω resistor?

$$i_{1\Omega} = i_{2\Omega} = 6 \text{ A}$$

$I_{1\Omega} = \underline{6.00} \text{ A}$

c. What is the current in the 6.00Ω resistor?

$$i_{6\Omega} = \frac{V}{R_{6\Omega}} = \frac{18.0 \text{ V}}{6 \Omega} = 3 \text{ A}$$

$I_{6\Omega} = \underline{3.00} \text{ A}$

d. Calculate the power dissipated by each resistor

$$P = I^2 R \quad P_1 = (6 \text{ A})^2 1 \Omega = 36 \text{ W}$$

$$P_2 = (6 \text{ A})^2 2 \Omega = 72 \text{ W}$$

$$P_3 = (3 \text{ A})^2 6 \Omega = 54 \text{ W}$$

$P_{1\Omega} = \underline{36} \text{ W}$

$P_{2\Omega} = \underline{72} \text{ W}$

$P_{6\Omega} = \underline{54} \text{ W}$

e. Calculate the power delivered by the battery.

$$I_{battery} = 6 \text{ A} + 3 \text{ A} = 9 \text{ A} \quad P_{battery} = VI = (18 \text{ V})(9 \text{ A})$$

$P_{battery} = \underline{162} \text{ W}$

15 points


3. An R-C circuit is shown in the figure to the right.

a. Calculate the time constant for this circuit.

$$\frac{1}{R_{eq}} = \frac{1}{2 \text{ k}\Omega} + \frac{1}{3 \text{ k}\Omega} + \frac{1}{6 \text{ k}\Omega} = \frac{6}{6 \text{ k}\Omega} \Rightarrow R_{eq} = 1 \text{ k}\Omega$$

$$C_{eq} = 5 \mu\text{F} + 5 \mu\text{F} = 10 \mu\text{F} \quad \tau = R_{eq} C_{eq} = (1 \times 10^3 \Omega)(10 \times 10^{-6} \text{ F})$$

$$\tau = \underline{10 \text{ ms}}$$

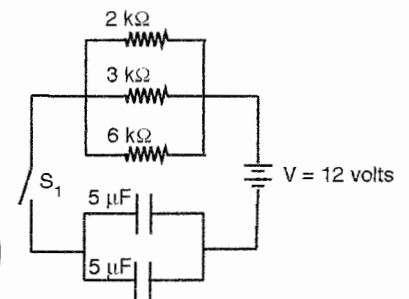

$$\tau = \underline{10} \text{ ms}$$

- b. At what time do the capacitors reach 90% of their final charge?

$$Q = Q_f (1 - e^{-t/RC}) \Rightarrow 0.90 Q_f = Q_f (1 - e^{-t/RC})$$

$$0.90 = 1 - e^{-t/RC} \Rightarrow e^{-t/RC} = \frac{1}{10} \quad -\frac{t}{RC} = \ln\left(\frac{1}{10}\right) \Rightarrow t = RC \ln(10)$$

$$t = 10 \text{ ms} \ln(10) = 23.0 \text{ ms}$$

$$t = \underline{23.0} \text{ ms}$$

- c. What is the instantaneous power delivered by the battery at $t = 20 \text{ ms}$?

$$P = VI \quad \text{where } I = I_0 e^{-t/RC} \quad \text{where } I_0 = \frac{V}{R_{eq}} = 12 \text{ mA}$$

$$I = 12 \text{ mA} e^{-20/10} \quad I = 1.62 \text{ mA} \quad P = VI = (12 \text{ V})(1.62 \text{ mA})$$

$$P_{\text{battery}} = \underline{19.5 \times 10^{-3}} \text{ W}$$

10 points

4. A proton traveling at $2/3$ of the speed of light enters a region of homogeneous magnetic field (1.30 T). If the velocity vector is perpendicular to the direction of the magnetic field,

- a) Calculate the radius of curvature of the proton.

$$R = \frac{mv}{qB} = \frac{(1.67 \times 10^{-27} \text{ kg}) \frac{2}{3} (3.0 \times 10^8 \text{ m/s})}{(1.602 \times 10^{-19} \text{ C})(1.30 \text{ T})} = 1.60 \text{ m}$$

$$R = \underline{1.60} \text{ cm}$$


- b) Calculate the frequency of the orbiting proton.

$$v = R\omega \quad \omega = \frac{v}{R} = \frac{v q B}{mv} = \frac{qB}{m} \quad \omega = 2\pi f$$

$$f = \frac{\omega}{2\pi} = \frac{qB}{2\pi m} = \frac{(1.602 \times 10^{-19} \text{ C})(1.30 \text{ T})}{2\pi (1.67 \times 10^{-27} \text{ kg})} = 1.98 \times 10^7 \text{ s}^{-1} \quad f = \underline{1.98 \times 10^7} \text{ sec}^{-1}$$

15 points

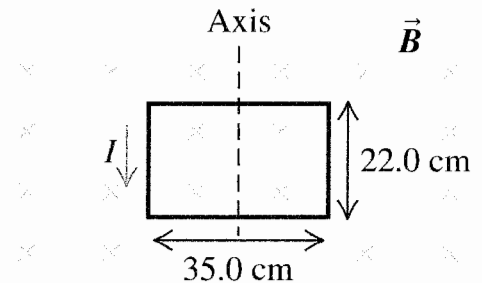5. A rectangular coil of wire, 22.0 cm by 35.0 cm and carrying a current of 1.40 A, is oriented with the plane of its loop perpendicular to a uniform 1.50-T magnetic field, as shown in the figure. If the coil is rotated through a 30.0° angle about the axis shown, the left side coming out of the plane of the figure and right side going into the plane,



$$\mu = \underline{0.108} \text{ A}\cdot\text{m}^2$$

- a. Calculate the magnetic dipole moment for this current loop.

$$\mu = IA = 1.40 \text{ A} (35 \times 22) \times 10^{-4} \text{ m}^2 = 0.108 \text{ A}\cdot\text{m}^2$$

$$\vec{\mu} = (\sin 30^\circ \hat{i} + \cos 30^\circ \hat{k}) (0.108 \text{ A}\cdot\text{m}^2)$$

- b. Calculate the torque vector. (Assume x is to the right and y is up.)

$$\vec{\tau} = \vec{\mu} \times \vec{B} = \begin{vmatrix} \hat{i} & \hat{j} & \hat{k} \\ \sin 30^\circ & 0 & \cos 30^\circ \\ 0 & 0 & -1.50 \end{vmatrix} (0.108 \text{ A}\cdot\text{m}^2) = \left[\hat{i} (0) - \hat{j} \left(\frac{1}{2} (-1.50) \right) + \hat{k} (0) \right] \times (0.108 \text{ A}\cdot\text{m}^2)$$

$$\vec{\tau} = (8.10 \times 10^{-2} \text{ N}\cdot\text{m}) \hat{j}$$

$$\vec{\tau} = \underline{0} \hat{i} + \underline{8.10 \times 10^{-2}} \hat{j} + \underline{0} \hat{k} \text{ N}\cdot\text{m}$$

- c. Calculate the potential energy


$$U = -\vec{\mu} \cdot \vec{B} = -\mu B \cos 30^\circ = -(0.108 \text{ A}\cdot\text{m}^2)(1.50 \text{ T}) \cos 30^\circ$$

$$U = -0.140 \text{ J}$$

$$U = \underline{-0.140} \text{ J}$$

15 points

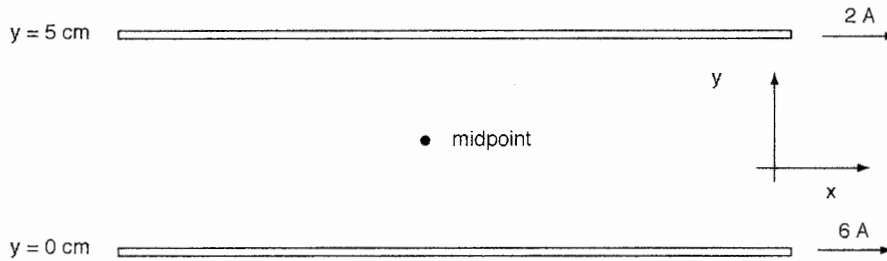6. Two infinitely long currents (shown in the figure below) are parallel and separated by 5.00 cm in a vacuum.



a. Calculate the magnetic field at a midpoint between the two wires.

$$B = \frac{\mu_0 I}{2\pi r} \quad \vec{B}_{2A} = \frac{\mu_0 (2A)}{2\pi (0.025)} (-\hat{k}) = \frac{4\pi \times 10^{-7} (2A)}{2\pi (0.025)} (-\hat{k}) = (-1.60 \times 10^{-5} \text{ T}) \hat{k}$$

$$\vec{B}_{6A} = \frac{\mu_0 (6A)}{2\pi (0.025)} (\hat{k}) = \frac{4\pi \times 10^{-7} (6A)}{2\pi (0.025)} \hat{k} = (+4.80 \times 10^{-5} \text{ T}) \hat{k} \quad \boxed{3.20 \times 10^{-5} \text{ T}}$$

$$\vec{B} = (0 \hat{i} + 0 \hat{j} + 3.20 \times 10^{-5} \hat{k}) \text{ T}$$

b. At what location in y is the magnetic field equal to zero?

$$B_{6A} = \frac{\mu_0 I_{6A}}{2\pi y} \quad B_{2A} = \frac{\mu_0 I_{2A}}{2\pi (5-y)} \quad B_{\text{TOTAL}} = B_{6A} - B_{2A} = 0$$

$$\frac{\mu_0 6A}{2\pi y} - \frac{\mu_0 2A}{2\pi (5-y)} = 0 \quad \frac{6}{y} - \frac{2}{5-y} = 0 \quad \rightarrow \frac{y}{3} = 5-y \rightarrow \frac{4}{3}y = 5 \quad y = \frac{15}{4} \text{ cm}$$

$$y = \underline{3.75} \text{ cm}$$

c. Calculate the force per unit length between the two current-carrying wires.

$$\frac{F}{L} = \frac{\mu_0 I_{2A} I_{6A}}{2\pi r} = \frac{\mu_0 (2A)(6A)}{2\pi (0.05)} = \frac{4\pi \times 10^{-7} (12)}{2\pi (0.05)} = \boxed{4.80 \times 10^{-5} \frac{\text{N}}{\text{m}}}$$

d. Is the force attractive or repulsive? (circle one)

$$\vec{F} = I \vec{L} \times \vec{B}$$